

Test Friday, 11/18



Electrostatics

Circuits

## • Equivalent Resistance:

- Resistors control current
- $V = IR$
- We want to know much current, so we need to know equivalent resistance

### - Series

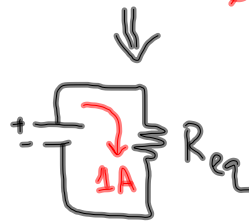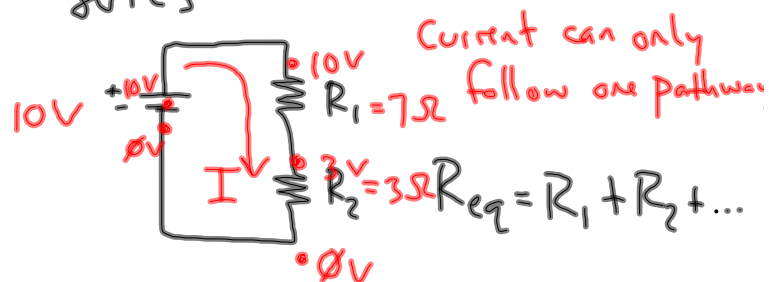

$$V_{total} = I_{total} R_{eq}$$

$$I_{total} = \frac{V_{total}}{R_{eq}}$$

$$= \frac{10V}{10\Omega}$$

$$= 1A$$



- Voltage drop  $\rightarrow$  how much potential is used in each resistor

### - Kirchhoff's Laws:

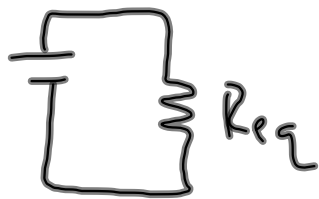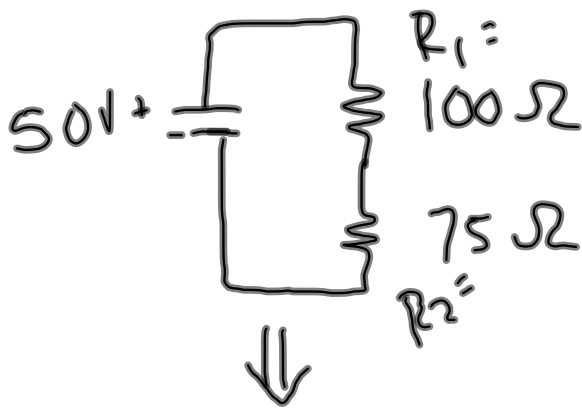1. All voltage is used around a loop.
2. Current into a junction equals sum of currents out of the junction.

$$V_1 = I_{total} R_1 \quad V_2 = I_{total} R_2$$

$$= (1A)(7\Omega) \quad = (1A)(3\Omega)$$



$$R_{eq} = R_1 + R_2$$

$$= 175 \Omega$$

$$V_{total} = I_{total} R_{eq}$$

$$I_{total} = \frac{V_{total}}{R_{eq}}$$

$$= \frac{50 \text{ V}}{175 \Omega}$$

$$= 0.286 \text{ A}$$

$$V_1 = I_{total} R_1$$

$$= (.286 \text{ A})(100 \Omega)$$


$$= 28.6 \text{ V}$$

$$V_2 = I_{total} R_2$$

$$= (.286 \text{ A})(75 \Omega)$$


$$= 21.4 \text{ V}$$

- Parallel:

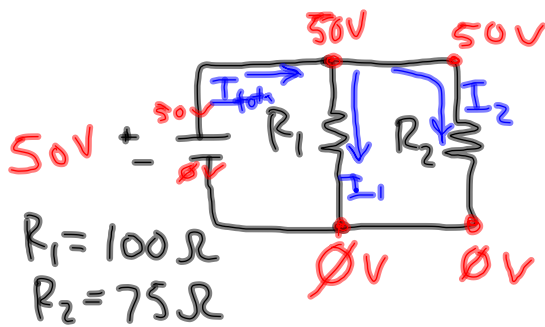

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$I_{total} = I_1 + I_2$$

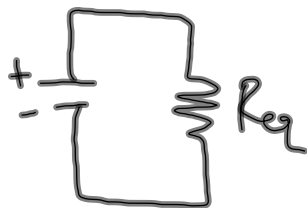

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \left[ \frac{1}{100\Omega} + \frac{1}{75\Omega} \right]^{-1}$$

$$V_{total} = I_{total} R_{eq}$$

$$= 42.9\Omega$$

$$I_{total} = \frac{V_{total}}{R_{eq}}$$

$$= \frac{50V}{42.9\Omega}$$

$$= 1.17A$$

$$V_{total} = I_1 R_1$$

$$I_1 = \frac{V_{total}}{R_1}$$

$$= \frac{50V}{100\Omega}$$


$$= 0.5A$$

$$V_{total} = I_2 R_2$$


$$I_2 = \frac{V_{total}}{R_2}$$

$$= \frac{50V}{75\Omega}$$


$$= .67A$$

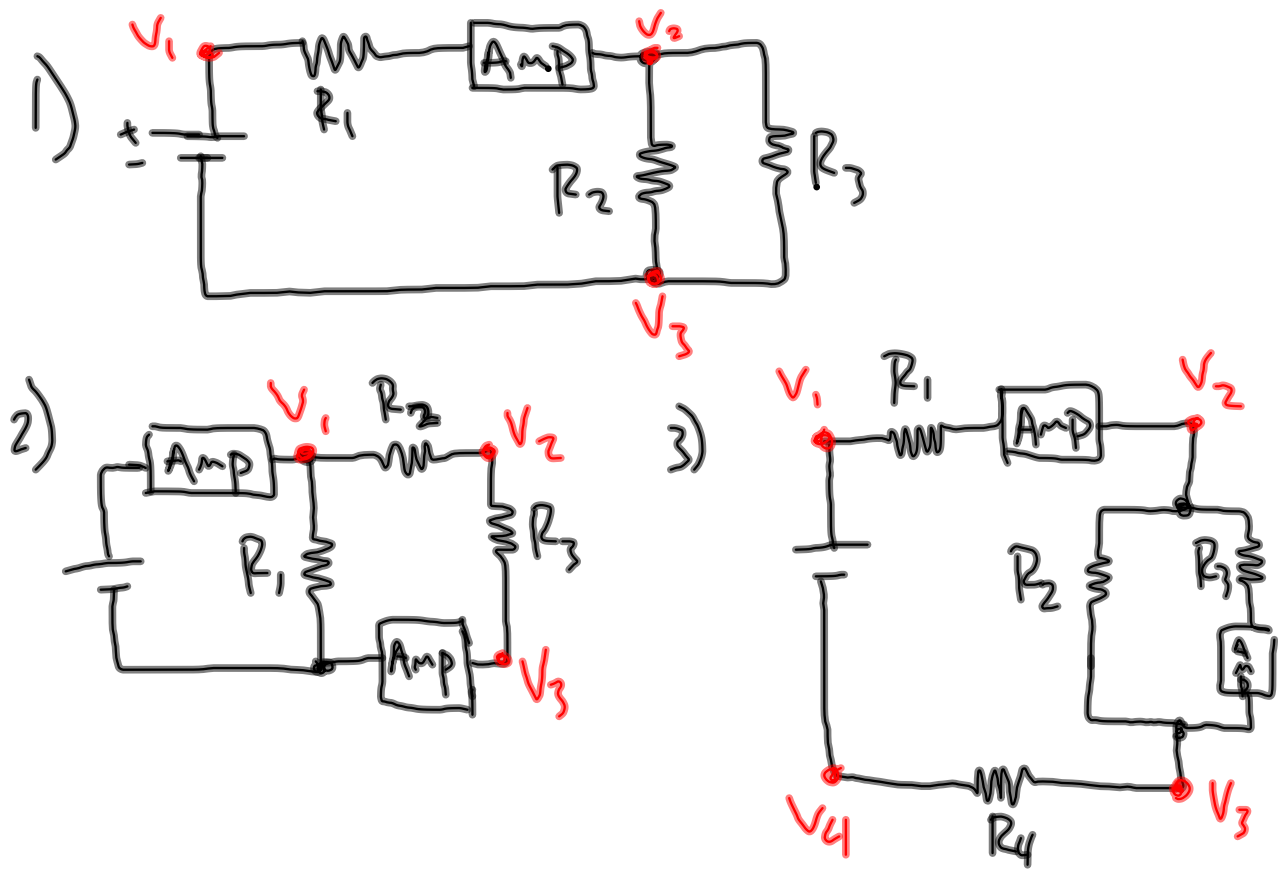

- Reducing Schematics:

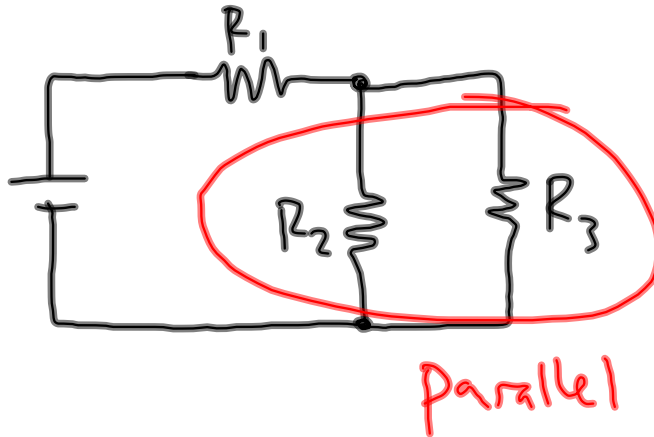

Start w/farthest  
away resistor

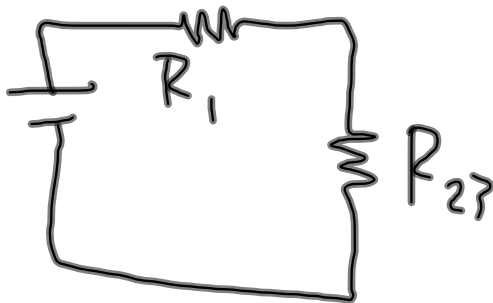

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

